

a) What determines the voltage V_X in figure 1? Consider $V_{eff,M1} = V_{eff,M2} = V_{eff,M3} = 100\text{mV}$

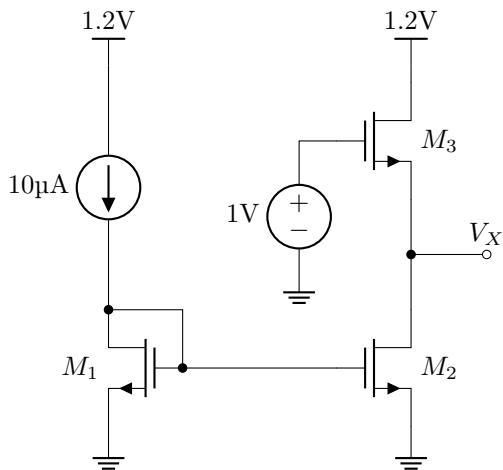


Figure 1