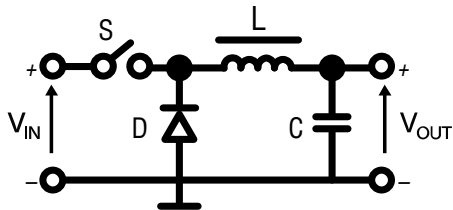


Non-isolated, non-inverting topologies, output voltage at same polarity as input.



### Step-down or Buck converter

$$0 \leq V_{OUT} \leq V_{IN} \quad V_{OUT} = d \cdot V_{IN}$$

Simple step down circuit with single switch (FET) and storage element (Inductor). The output capacitor  $C$  is needed to remove significant output ripple. Synchronous version replaces  $D$  with second FET.

Ref: <https://www.mouser.com/applications/power-supply-topology-buck/>

### Step-up or Boost converter

$$V_{OUT} \geq V_{IN} \quad V_{OUT} = V_{IN} / (1-d)$$

Simple step up circuit with single switch and storage element. The output capacitor  $C$  is needed to remove significant output ripple. Synchronous version replaces  $D$  with second FET

